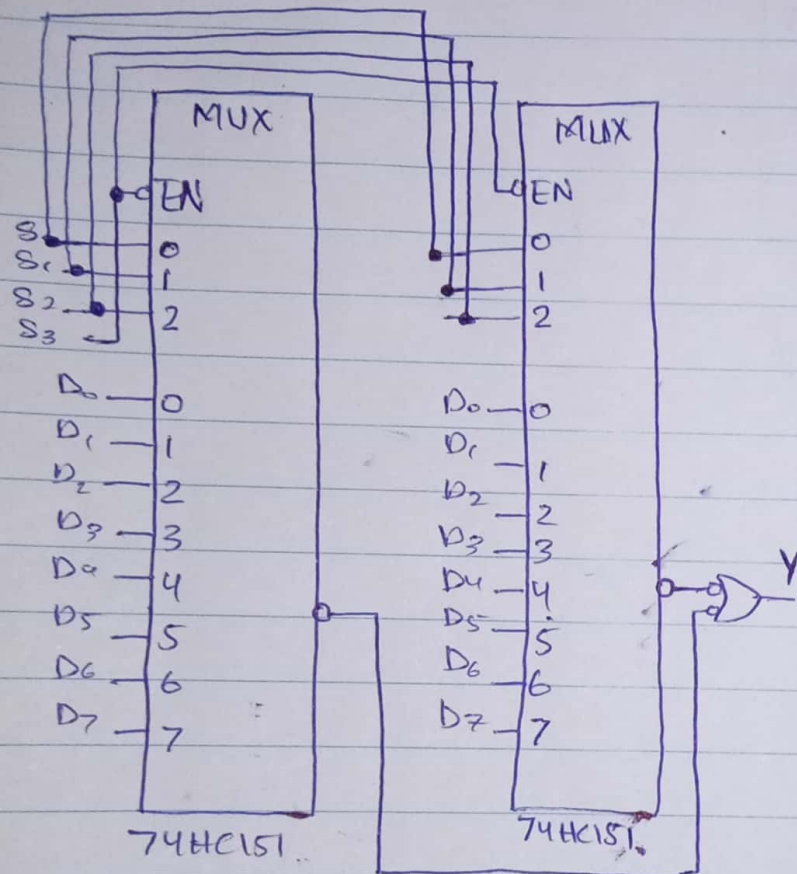


Assignment #04

Example # E-15



16-input multiplexer

Example # 7-11

SOLUTIONS-

Arbitrarily select $R_{EXT} = 39K\Omega$
& calculate the necessary
capacitance

$$t_w = 0.7 R_{EXT} C_{EXT}$$


$$C_{EXT} = \frac{t_w}{0.7 R_{EXT}}$$

where C_{EXT} is in PF, R_{EXT}
is in K Ω & t_w is in ns
Since $100ms = 1 \times 10^8 ns$

$$C_{EXT} = \frac{1 \times 10^8 ms}{0.7 (39K\Omega)}$$

$$= 3.66 \times 10^{-6} pF$$

$$C_{EXT} = 3.66 \mu F$$

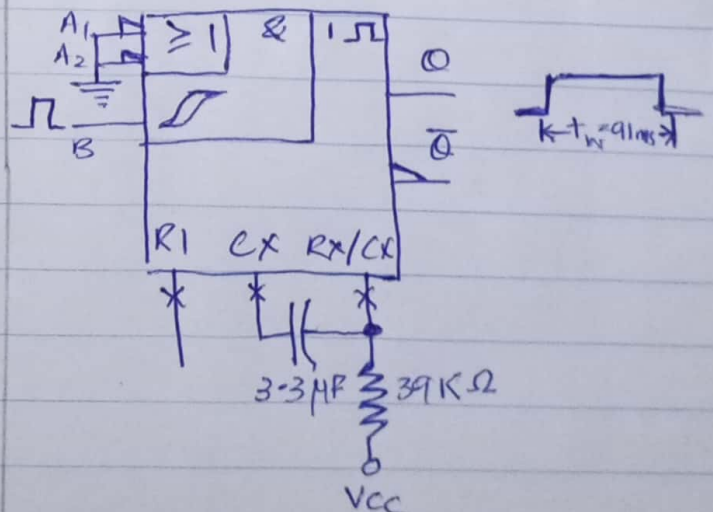

22K-4187

Example # 7-12

SOLUTION:-

Assume a value of $C_{EXT} = 500 \text{ pF}$ and then solve for R_{EXT} . The pulse width must be expressed in ns & C_{EXT} in pF & R_{EXT} in Ω .

$$t_W = 0.32 R_{EXT} C_{EXT} \left(1 + \frac{0.7}{R_{EXT}} \right)$$

$$t_W = 0.32 R_{EXT} C_{EXT} + 0.7 \left(\frac{0.32 R_{EXT} C_{EXT}}{R_{EXT}} \right)$$

$$t_W = 0.32 R_{EXT} C_{EXT} + 0.7(0.32) C_{EXT}$$

$$R_{EXT} = \frac{t_W - 0.7(0.32) C_{EXT}}{0.32 C_{EXT}}$$

$$= \frac{t_W}{0.32 C_{EXT}} - 0.7$$

$$= \frac{1000 \text{ ns}}{0.32(500) \text{ pF}} - 0.7$$

$$R_{EXT} = 4.88 \text{ K}\Omega$$

Using standard value of 4.7 K Ω

22K-4187

Example # 7-13

SOLUTION:-

The pulse width is given by,

$$t_W = 1.1 R_1 C_1$$

$$= 1.1 (2.2 \text{ K}\Omega) (10.01 \text{ pF})$$

$$t_W = 24.2 \mu\text{s}$$

CHECK-UP Q.4

— (ANS#01) —

→ There are total 16 states in an 8-bit Johnson Counter.

— (ANS#02) —

The sequence is

Initially → 000

CLK-1 → 100

CLK-2 → 110

CLK-3 → 111

CLK-4 → 011

CLK-5 → 001

CLK-6 → 001

22K-4187